Pre-amp

朱启通

The first stage comp design




- Comp design
- Preamp design
- Autozero eliminate os

- The first stage comp choice, and spec analysis.
- current≤50uA, speed≥800MHZ, offset (3σ) ≤4mv, input
 reference noise (3σ) ≤1mv, common mode voltage=0.9V

Architecture

architecture—preamp+strongarm latch

 Decrease os of strongarm latch Introduce os of preamp



Strongarm latch design


Strongarm latch os≈4.735mv (σ)

Strongarm latch cycle=2.5ns

Strongarm latch current=14.5uA


Strongarm latch design

Circuits implementation

 

第一级比较器的设计

Stimuilate result

 

Strongarm latch offset mentor carlo 3σ =28.2m

Preamp design

Strongarm latch os≈4.76mv (σ)



Strongarm latch cycle=2.5ns



Strongarm latch current=14.5uA



The first stage comp design



- Comp design
- Preamp design
- Autozero eliminate os

Preamp design

Preamp gain=5


Preamp f-3db>1Ghz

Preamp current<24.5uA

architecture: fully different amp connecting diodes


Preamp design

Circuit implementation

 

第一级比较器的设计

• 仿真结果

 

Preamp gain=5.4

f-3db=1.5GGhz

第一级比较器的设计

• 利用oos技术消除preamp的offset

 


图 4.7 失调校准方法之 OOS

Offset 采样阶段: S3-5闭合, S1-2断开 Offset 消除阶段: S3-5断开, S1-2闭合

The first stage comp design



- Comp design
- Preamp design
- Autozero eliminate os

autozero

Offset capacitor


 


图 4.7 失调校准方法之 OOS

 

autozero

Offset capacitor

 


图 4.7 失调校准方法之 OOS




在offset 采样阶段,同时也是信号采样的阶段,采样阶段30ns,负载为存储offset电容, 折中考虑速度和精度和功耗取offset电容为120f

Considering speed, resolution and power, the offset c = 120f


autozero

Circuits implementation

 

Comp design

Stimulation result

 

offset=3.72mv (3 σ)

Thanks for attention